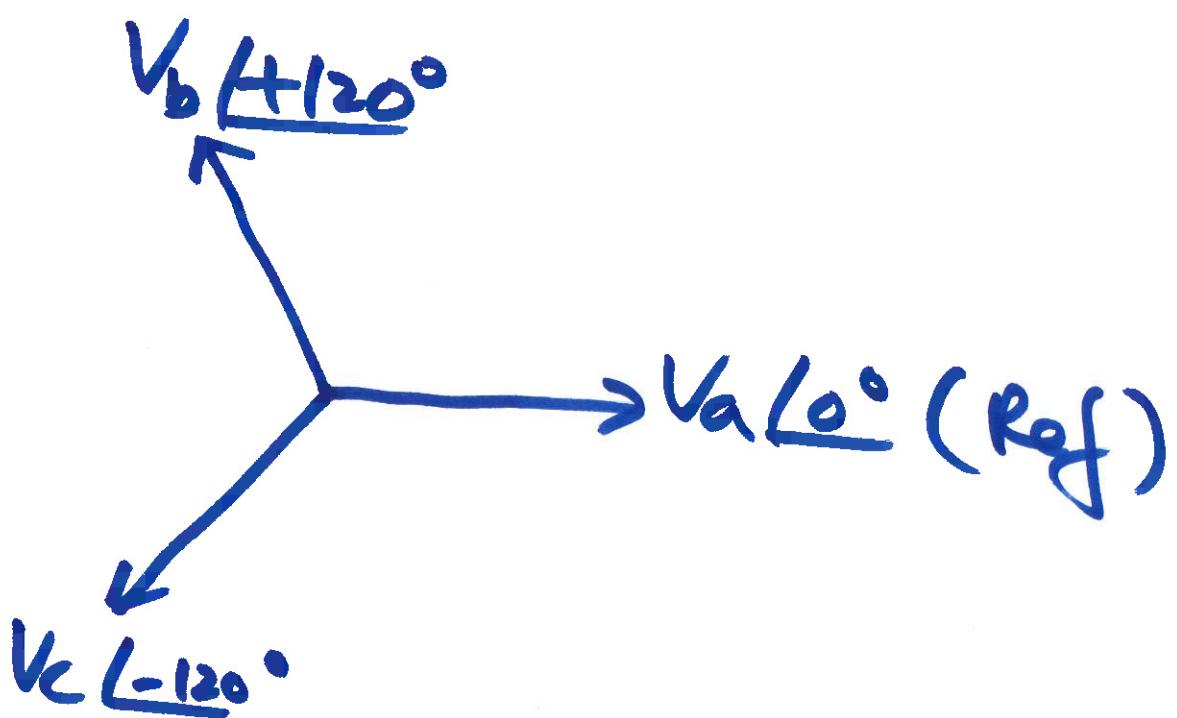


PPS - a, b, c




NPS - a, c, b

$\rightarrow V_a / 90^\circ$   
 $\rightarrow V_b / 90^\circ$   
 $\rightarrow k / 90^\circ$

ZPS




# Harmonic sequences

1-Phase

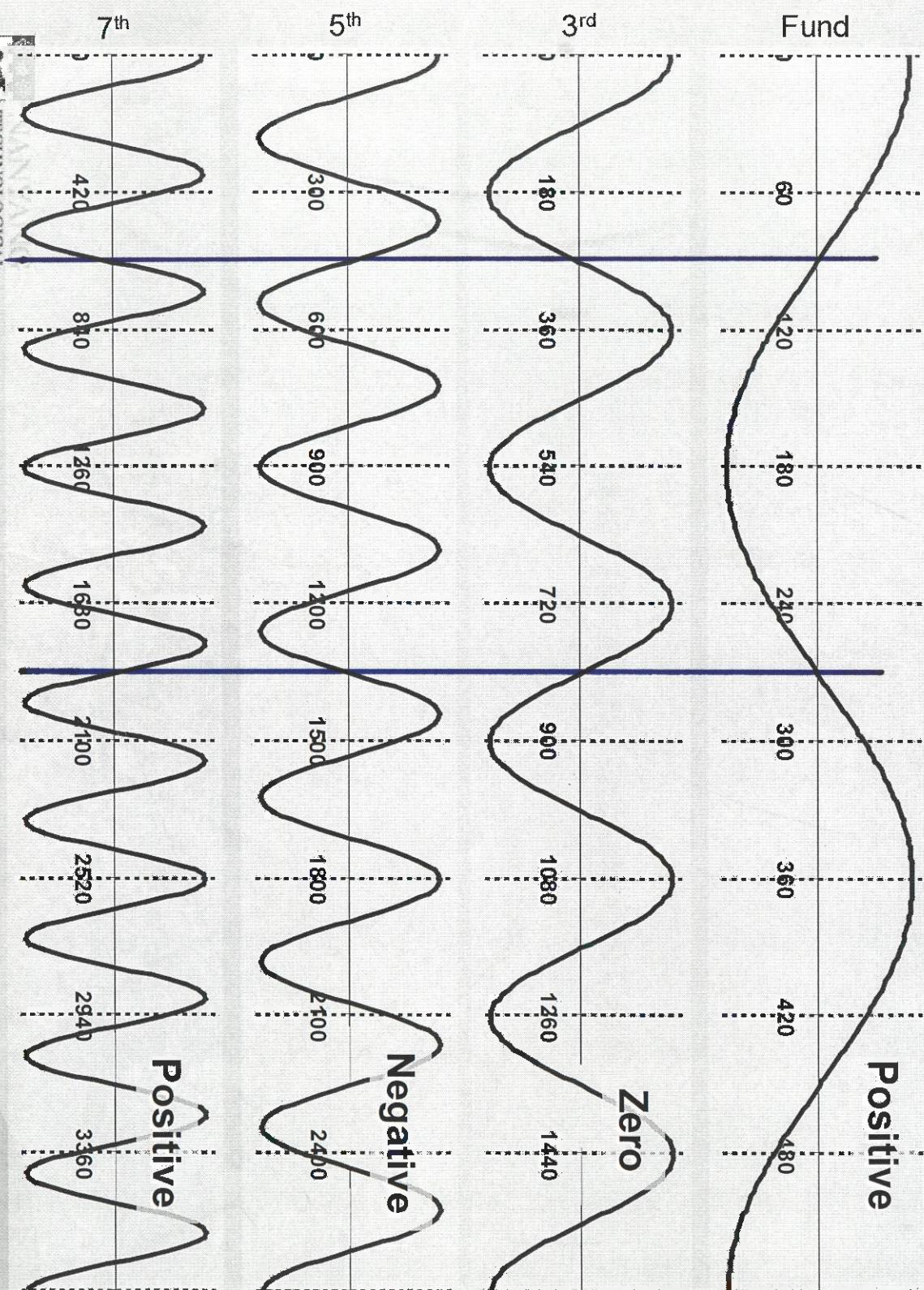


# Harmonic sequences

3-phase

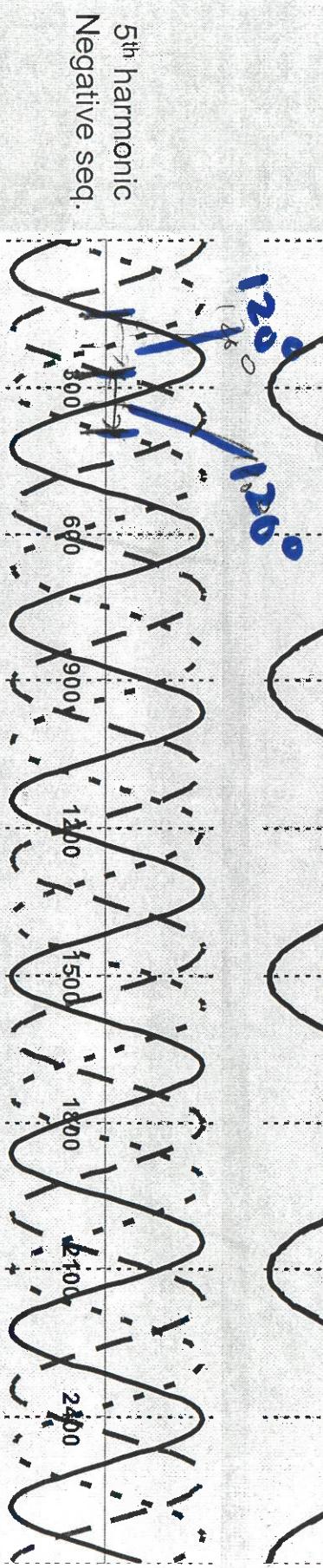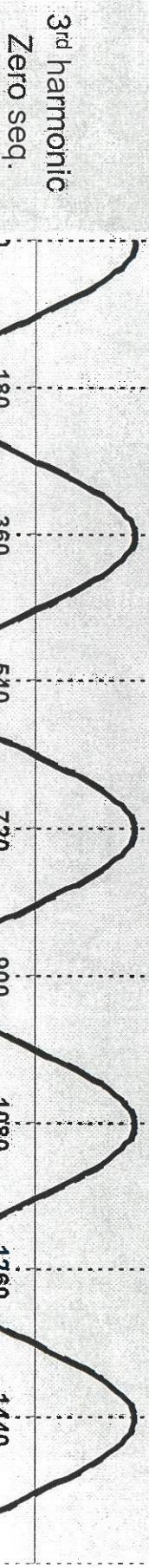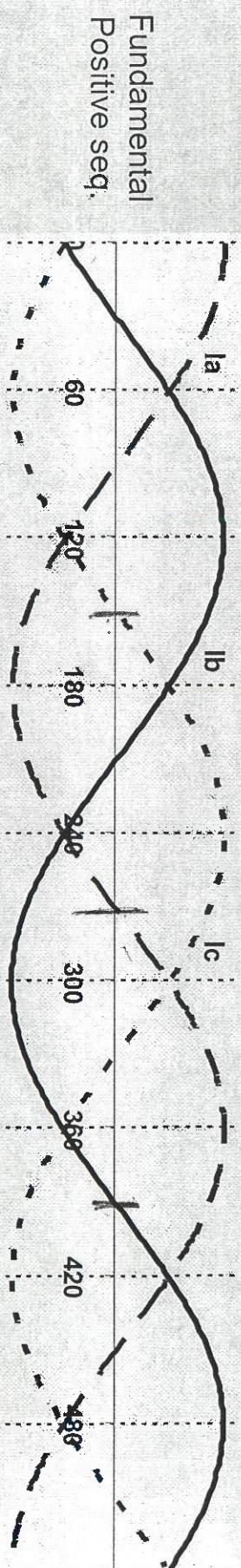

7<sup>th</sup> harmonic  
Positive seq.

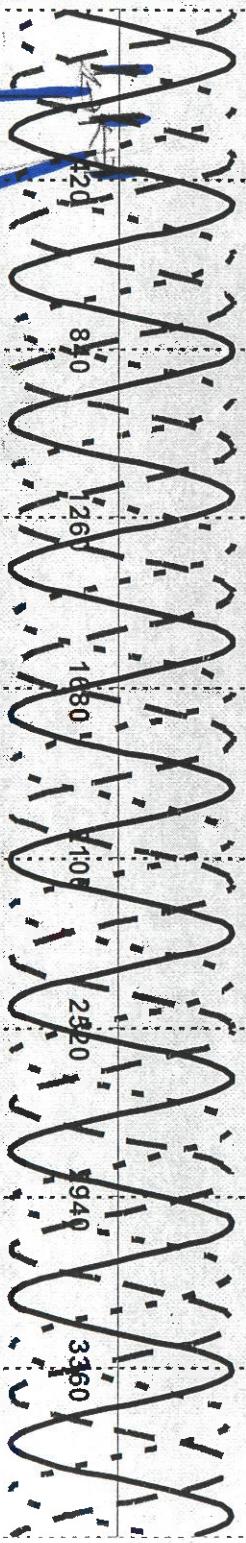


$$\downarrow X_{L,h} = 2\pi f h \downarrow L = x_{L,1} h$$

$$\downarrow X_{c,h} = \frac{1}{2\pi f h \uparrow c} = \frac{x_{c,1}}{h}$$

# Distribution Transformer

1 MVA

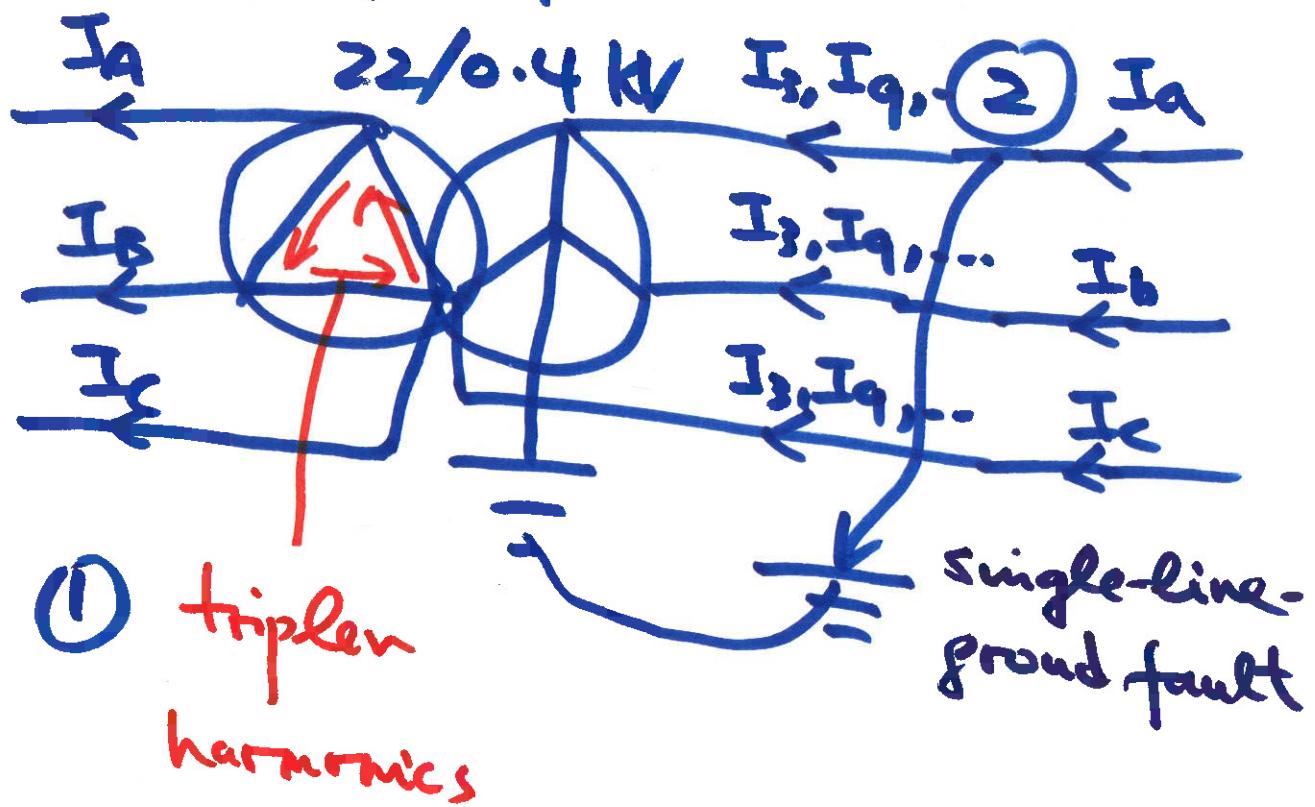

Complex Power


$$\bar{S} = \sqrt{3} V_L I_L \angle \phi$$
$$= S \angle \phi$$


$$S = \sqrt{3} V_L I_L$$

$$\therefore I_L = \frac{S}{\sqrt{3} V_L}$$

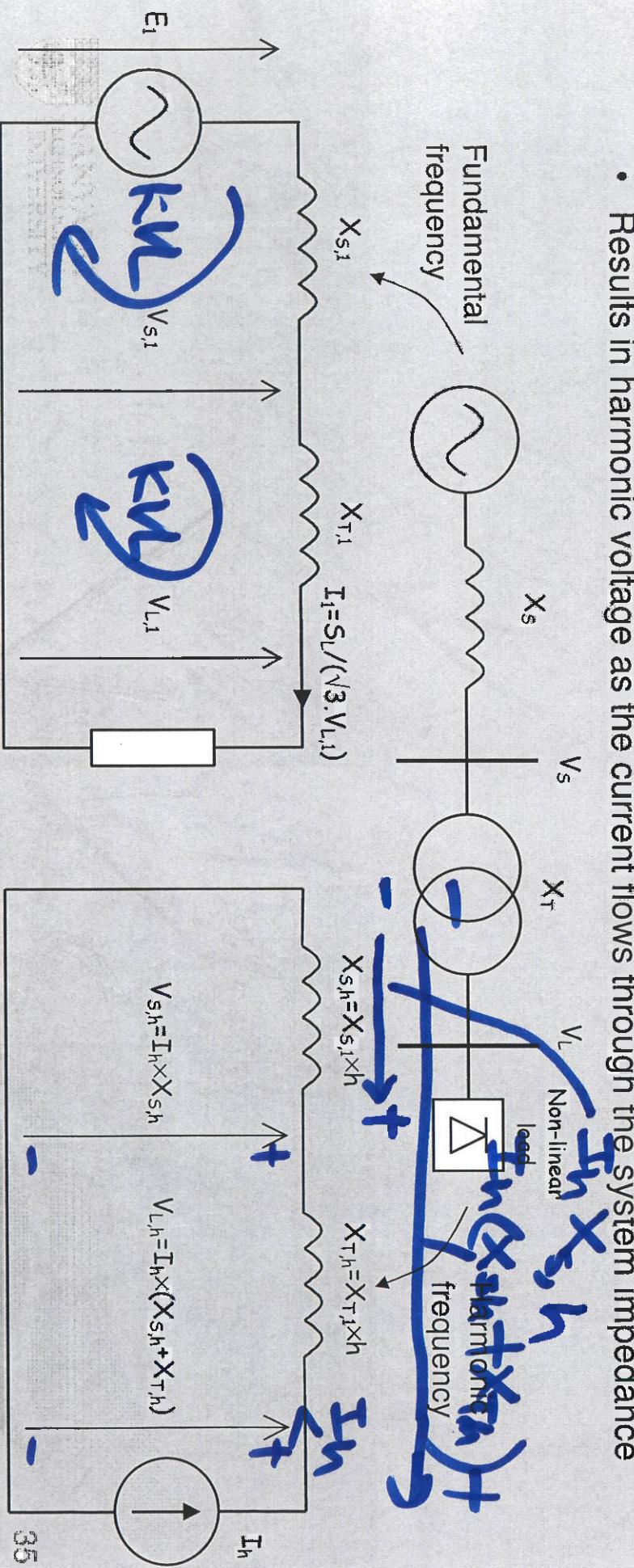
# Visualizing system response to harmonics

- System responds differently to currents and voltages of different frequencies
  - Separate individual harmonic responses from the fundamental response
  - At fundamental frequency, voltages are dependent on the voltage drops across system impedances due to the power or current flow as drawn by the load
  - At a harmonic frequency, non-linear load acts as harmonic current source, injecting harmonic current into the supply system
    - Results in harmonic voltage as the current flows through the system impedance



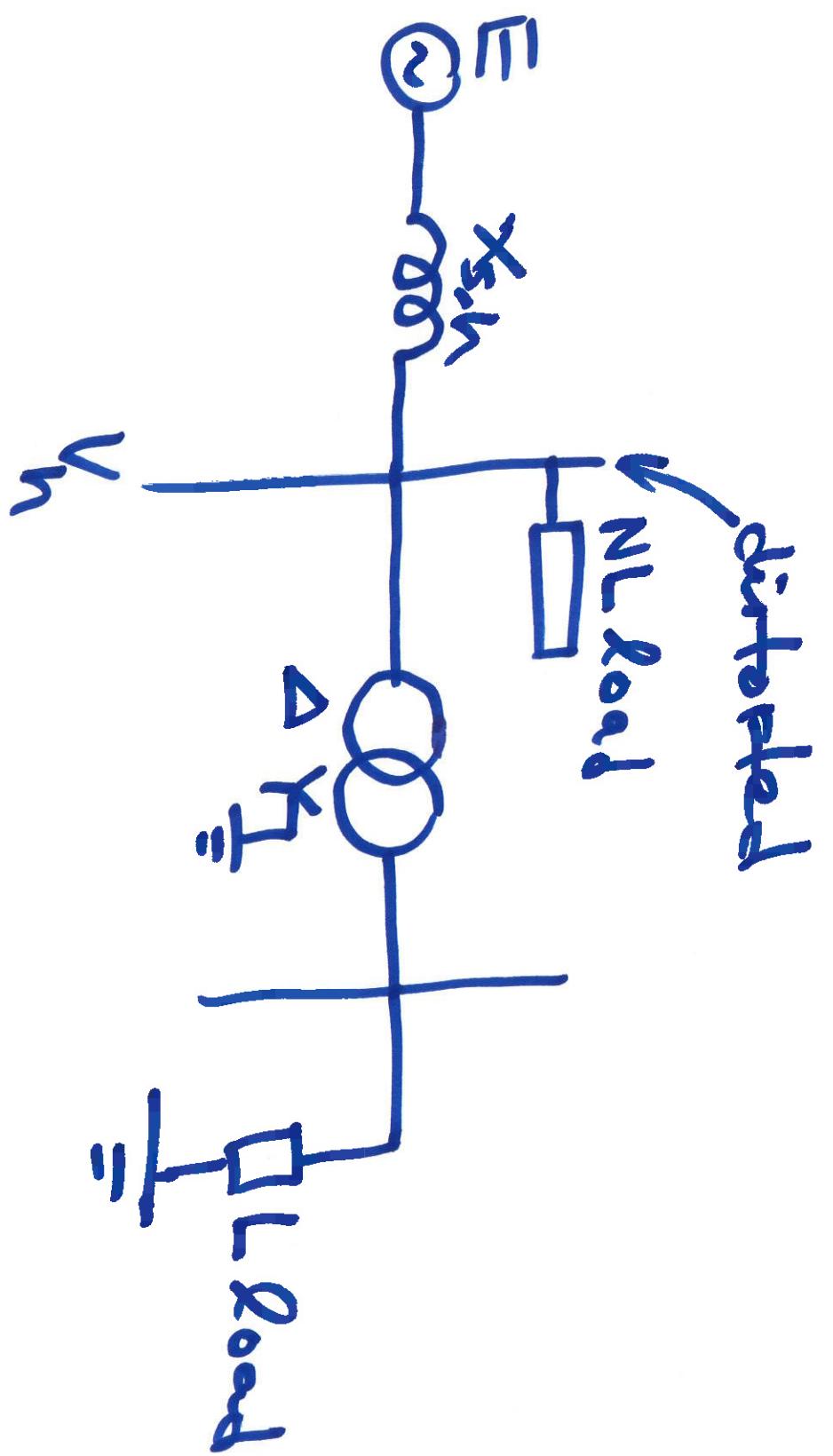

## Short-circuit Test

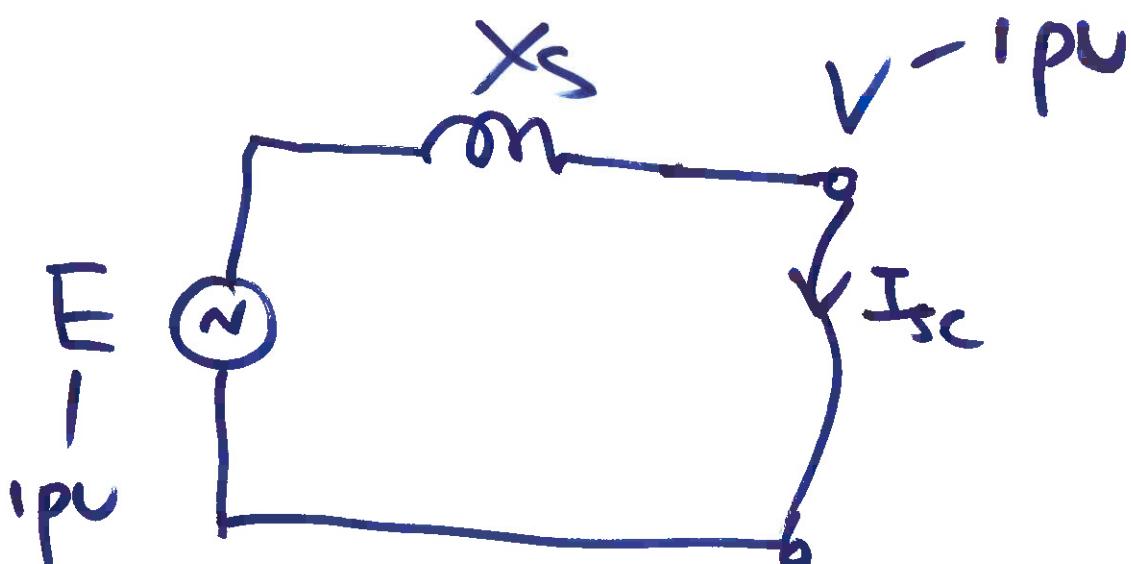

Short Circuit Capacity

$$SCC = V I_{sc} \quad \text{VA, kVA, MVA}$$

$$1 \text{ pu} = V E - 1 \text{ pu}$$



$$= \frac{E}{X_S}$$

$$= \frac{1}{X_S}$$

$$X_S = \frac{1}{SCC}$$


# Triplen harmonic voltages


$$\frac{\sqrt{3}}{2}$$

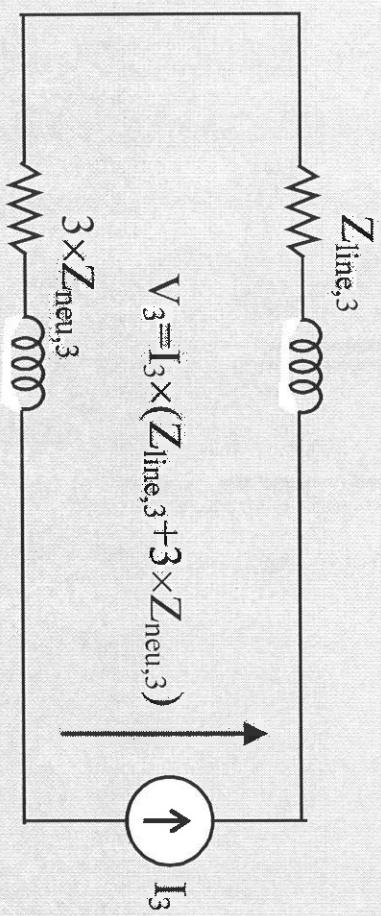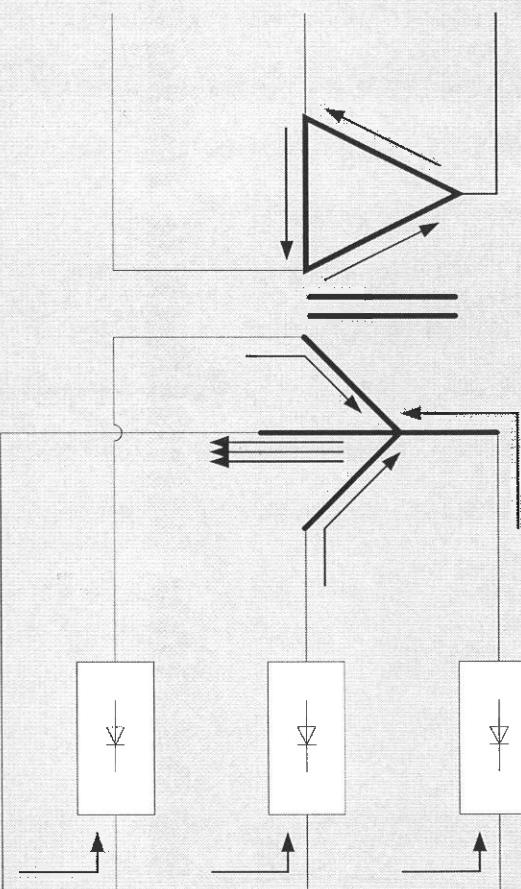

$$V_3 = I_3 Z_{\text{line},3} + 3 I_3 Z_{\text{neu},3}$$
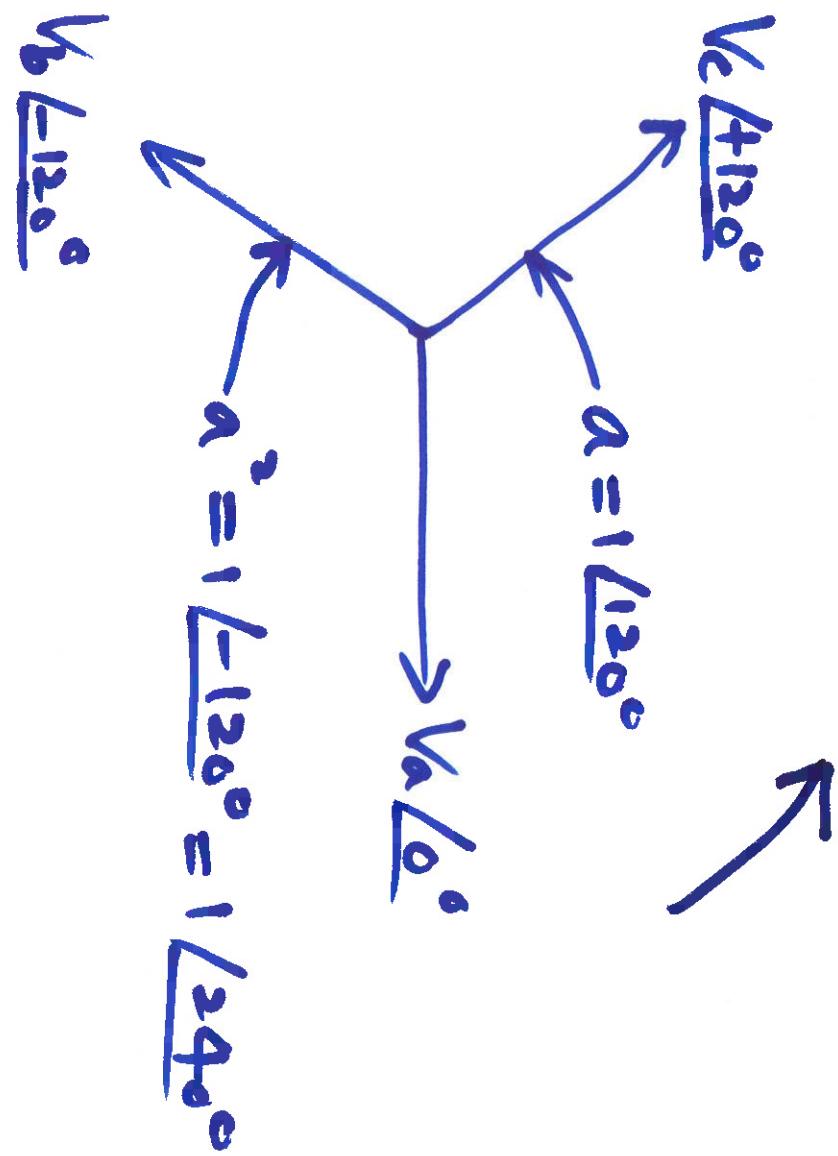
$$= I_3 (Z_{\text{line},3} + 3 Z_{\text{neu},3})$$



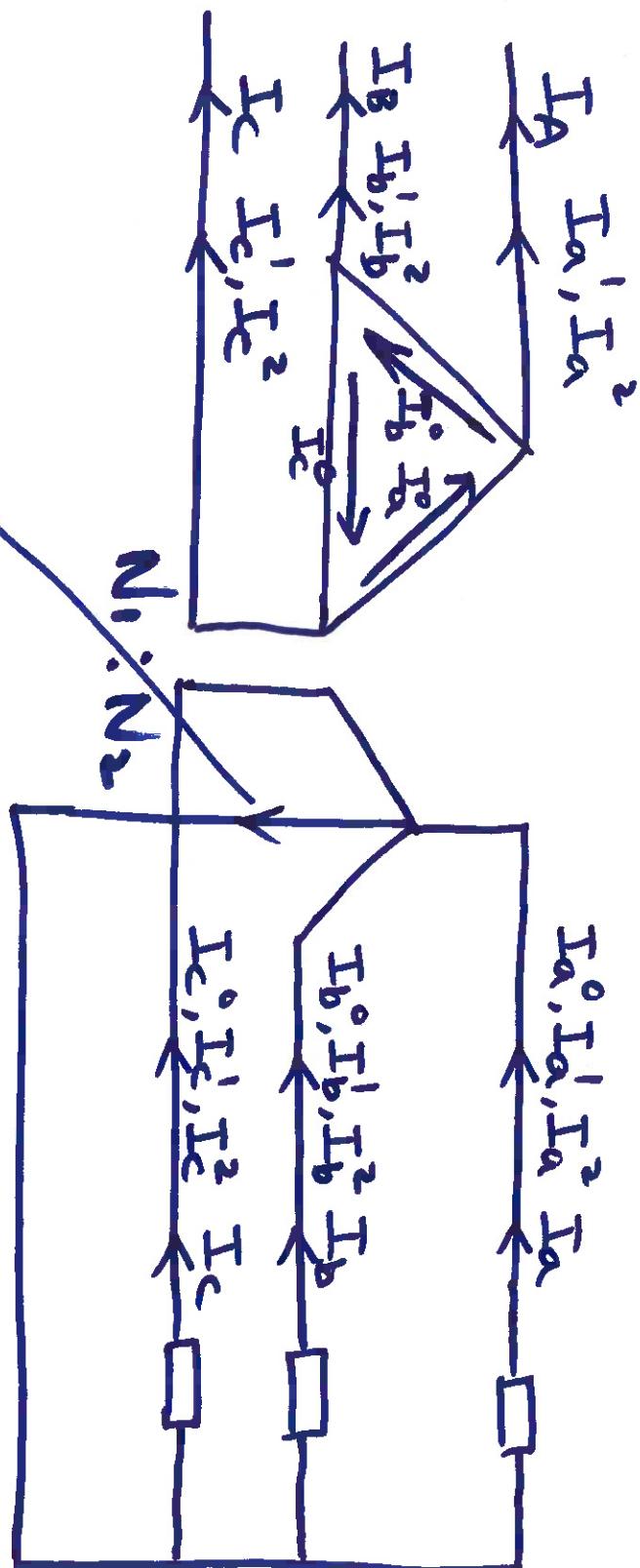


$$\begin{aligned}
 I_N &= I_a + I_b + I_c \\
 &= I_a^o + I_b^o + I_c^o = 3I_a^o
 \end{aligned}$$

$$I_A = \frac{I_a}{a} = \frac{I_a}{\frac{N_1}{N_2}} = \frac{N_2}{N_1} I_a$$

$$a = \frac{N_1}{N_2}$$
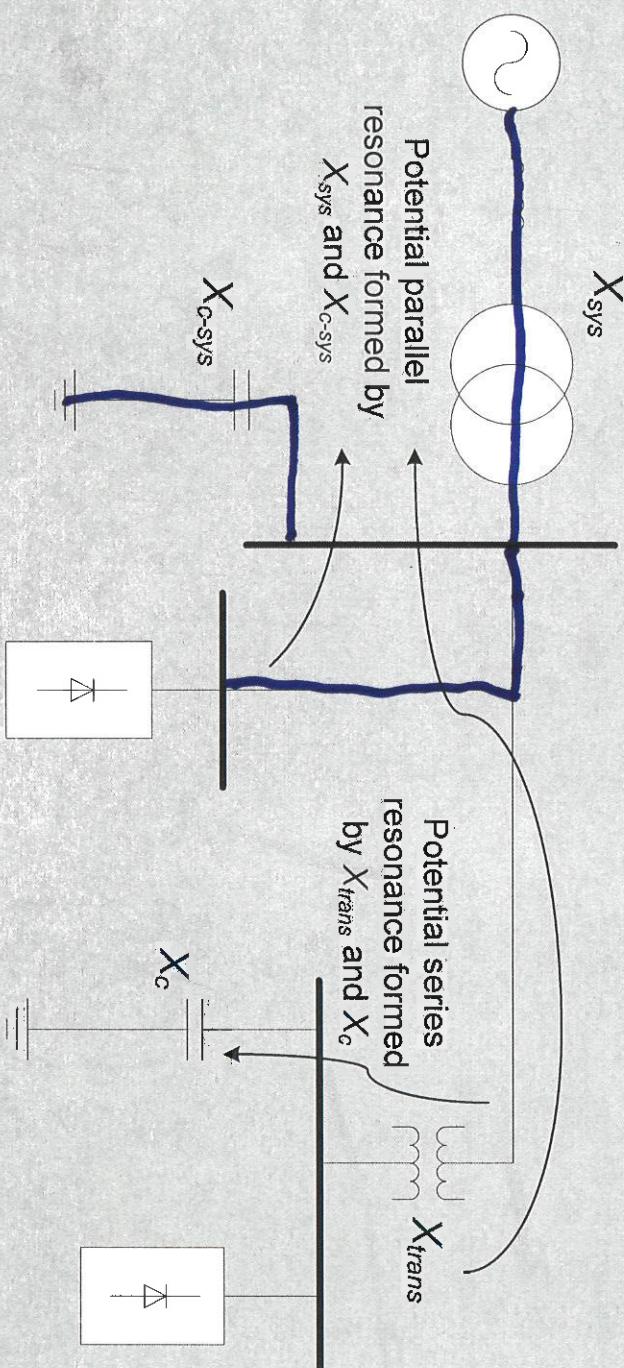
# Parallel and series resonances


- Resonance occurs when an inductive reactance equal to a capacitive reactance at or near a characteristic harmonic frequency
  - Parallel resonance involving supply system and substation capacitors or supply system with power factor correction capacitor
  - Series resonance made up of distribution transformer and power factor improvement capacitor



- A resonance point becomes problematic only when there is a harmonic source that excites (kick-starts) the resonance effect
- Harmonic frequency is close to or equal to the resonance frequency
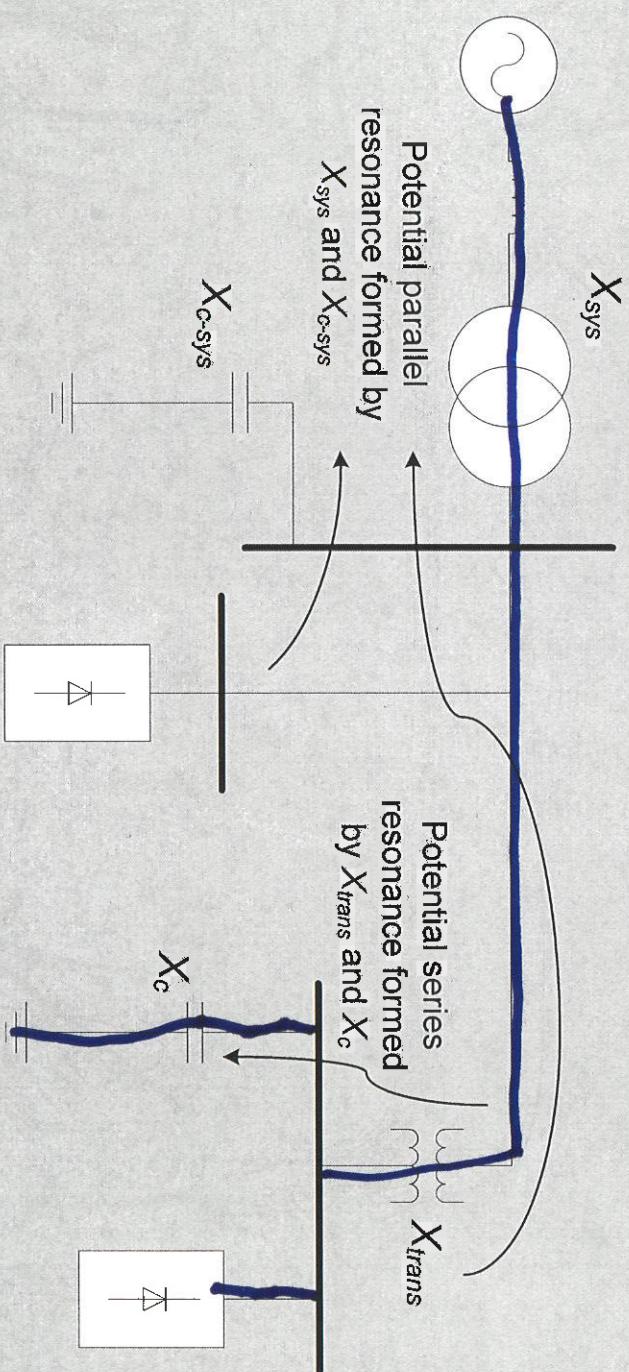
## Parallel and series resonances


- Resonance occurs when an inductive reactance equal to a capacitive reactance at or near a characteristic harmonic frequency
  - Parallel resonance involving supply system and substation capacitors or supply system with power factor correction capacitor
  - Series resonance made up of distribution transformer and power factor improvement capacitor



- A resonance point becomes problematic only when there is a harmonic source that excites (kick-starts) the resonance effect
- Harmonic frequency is close to or equal to the resonance frequency
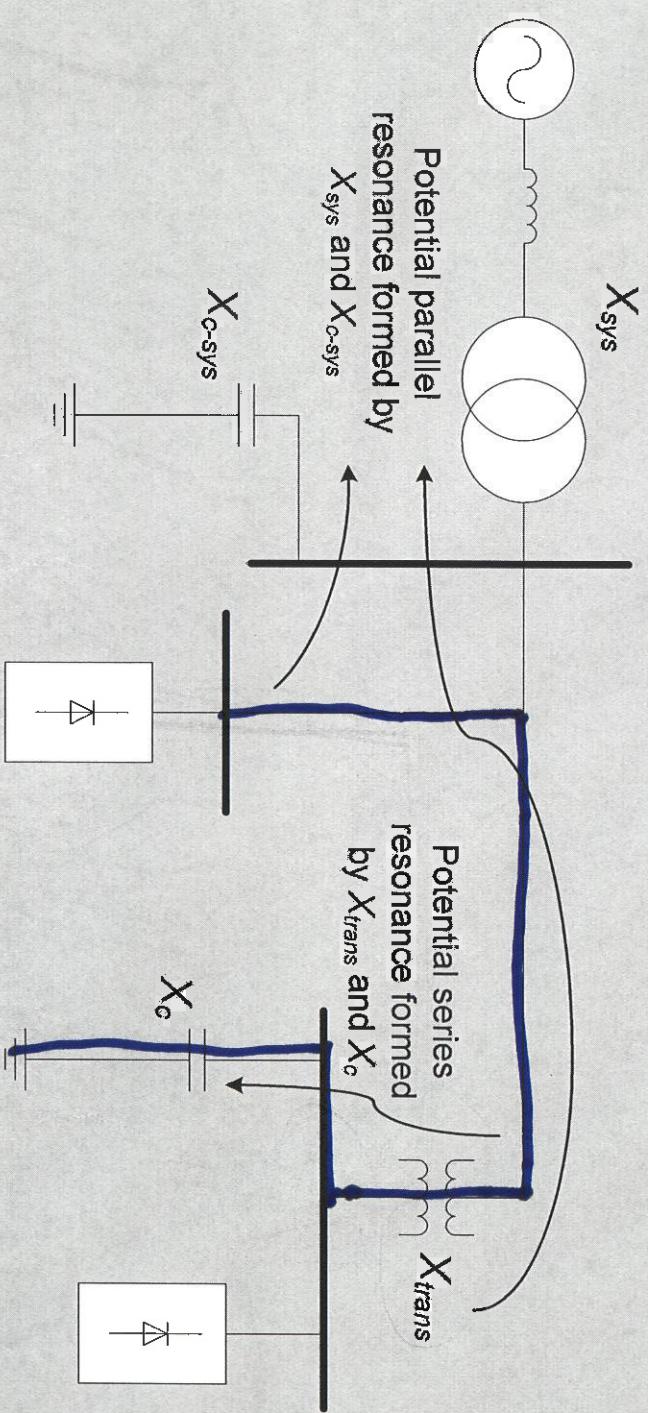
# Parallel and series resonances

- Resonance occurs when an inductive reactance equal to a capacitive reactance at or near a characteristic harmonic frequency
  - Parallel resonance involving supply system and substation capacitors or supply system with power factor correction capacitor
  - Series resonance made up of distribution transformer and power factor improvement capacitor



- A resonance point becomes problematic only when there is a harmonic source that excites (kick-starts) the resonance effect
- Harmonic frequency is close to or equal to the resonance frequency

At resonance

$$X_L = X_C$$

$$2\pi f L = \frac{1}{2\pi f C}$$

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

Resonance  
frequency

e.g. 150 Hz

$$x_{s,1} = 2\pi f L_s$$

$$x_{s,h} = 2\pi f h L_s$$

$$= h \underline{\underline{x}_{s,1}}$$

$$x_{T,1} = 2\pi f L_T$$


$$x_{T,h} = 2\pi f h L_T$$

$$= h \underline{\underline{x}_{T,1}}$$

$$x_{c,1} = \frac{1}{\omega_c} = \frac{1}{2\pi f c_1}$$

$$x_{c,h} = \frac{1}{2\pi f h c_1}$$
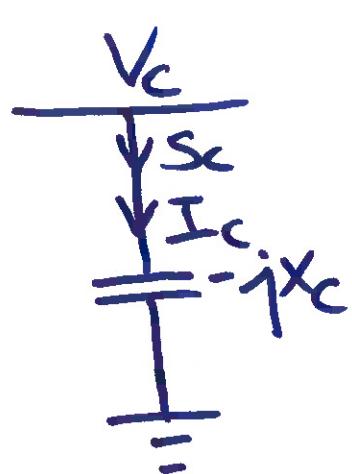
$$= \underline{\underline{\frac{x_{c,1}}{h}}}$$



$$Z_c = \frac{1}{j\omega c}$$

$$= \frac{1}{j j \omega c}$$

$$= -j \frac{1}{\omega c}$$

$$X_c = \frac{1}{\omega c}$$

$$= -j X_c$$

$$S_c = V_c I_c^*$$

$$= V_c \left( \frac{V_c}{-j X_c} \right)^* = \frac{V_c V_c^*}{j X_c}$$

$$= \frac{V_c^2}{j X_c} = -j \frac{V_c^2}{X_c}$$

$$= -j Q_c \quad | \text{ P.U}$$

$$Q_c = \frac{V_c^2}{X_c} \Rightarrow X_c = \frac{V_c^2}{Q_c}$$

S<sub>cap</sub>

$$\therefore X_c = \frac{1}{S_{cap}}$$

$$h = \sqrt{\frac{x_{\text{efund}}}{x_{\text{sfund}}}}$$

$$= \sqrt{\frac{\overline{s_{\text{cap}}}}{\overline{s_{\text{sec}}}}}$$

$$= \sqrt{\frac{s_{\text{sec}}}{s_{\text{cap}}}}$$

1.512

$$\frac{V_{ch}}{V_h} = \frac{j\omega C \cdot R_T}{(4\pi \times 10^{-6} \cdot 10^3) \cdot R_T} = -j \frac{\omega C}{4\pi \times 10^{-6}}$$

$2\pi f \times 5$

$$= \frac{-j 15.92}{j 2\pi \times 50 \times 5 \times 4\pi \times 10^{-6} \times 10^3}$$

$$Z = R_T + jX_{T,h} + (-jX_{C,h})$$


At resonance,  $X_{T,h} = X_{C,h}$

$\therefore Z = R_T$  (low impedance)
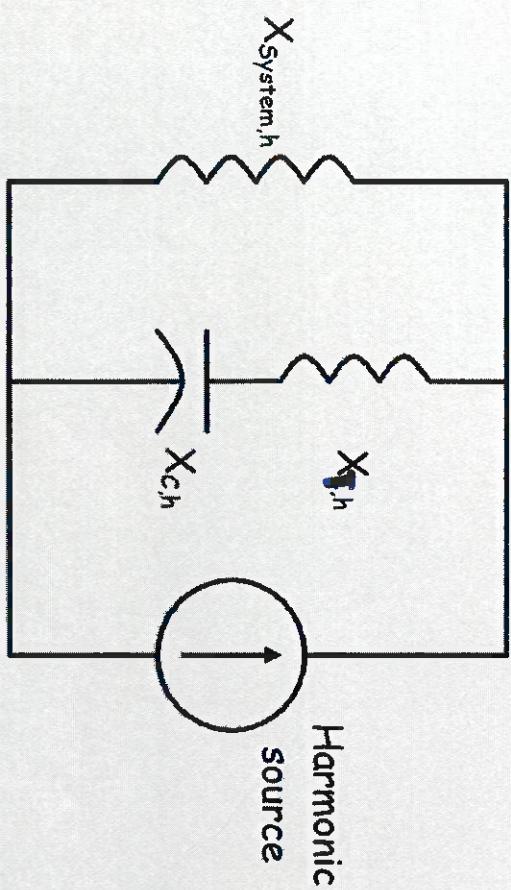
# Concurrent parallel and series resonances

- At frequency lower than the series resonant frequency,
  - The series branch of transformer inductive impedance and capacitor reactance becomes capacitive as  $X_c$  increases with decreasing frequency  $\cancel{X_C = \frac{1}{2\pi f C}}$
  - This branch will result in a parallel resonance with the system impedance (which is inductive) at a frequency slightly lower than the series resonant frequency

$$f_p = f_{fund} \sqrt{\frac{X_{C,fund}}{X_{S,fund} + X_{L,fund}}}$$



**Series resonance**

